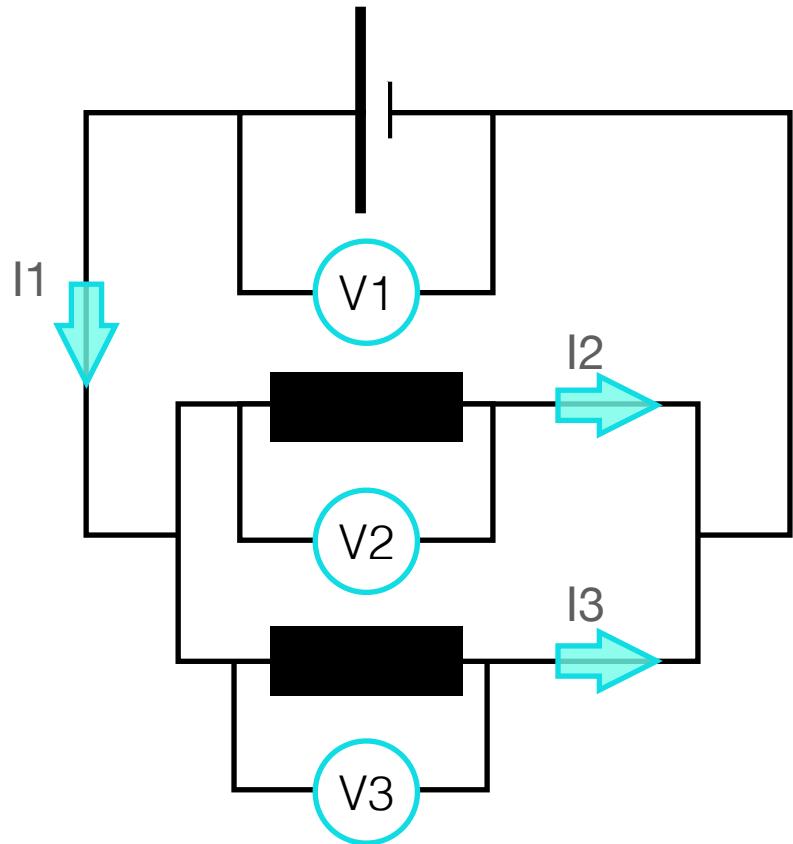


# series and parallel circuits



handmadescience.co.uk/



$I_1 =$  \_\_\_\_\_


$V_1 =$  \_\_\_\_\_

$I_2 =$  \_\_\_\_\_

$V_2 =$  \_\_\_\_\_

$I_3 =$  \_\_\_\_\_

$V_3 =$  \_\_\_\_\_

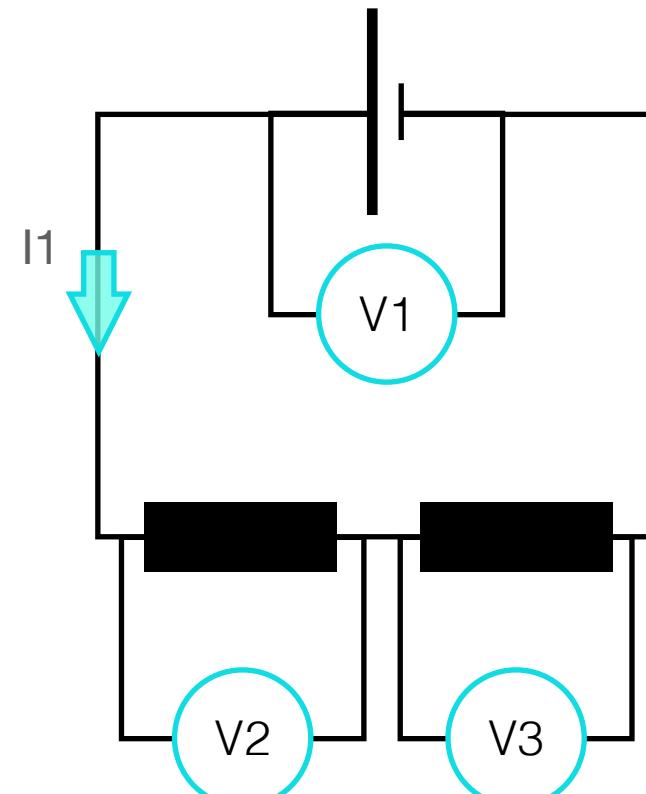

$I_1 =$  \_\_\_\_\_

$V_1 =$  \_\_\_\_\_

$V_2 =$  \_\_\_\_\_

$V_3 =$  \_\_\_\_\_